

## Simple Processor

This project was to implement a simple processor that can add, or, and 2-bit inputs. KEY0 is used store the values in the switches in a register. KEY1 is used to execute the instruction.

The instructions are:

Output A, output not A, output A+B, output A and B.

Inputs used: CLOCK\_50, SW, KEY

Outputs used: LED


Compilation Report:

| Flow Summary                       |  |
|------------------------------------|--|
| Flow Status                        | Successful - Tue Feb 17 20:23:56 2015      |
| Quartus II 64-Bit Version          | 14.1.0 Build 186 12/03/2014 SJ Web Edition |
| Revision Name                      | proce                                      |
| Top-level Entity Name              | proce                                      |
| Family                             | Cyclone IV E                               |
| Device                             | EP4CE22F17C6                               |
| Timing Models                      | Final                                      |
| Total logic elements               | 9 / 22,320 ( < 1 % )                       |
| Total combinational functions      | 5 / 22,320 ( < 1 % )                       |
| Dedicated logic registers          | 6 / 22,320 ( < 1 % )                       |
| Total registers                    | 6  |
| Total pins                         | 9 / 154 ( 6 % )                            |
| Total virtual pins                 | 0  |
| Total memory bits                  | 0 / 608,256 ( 0 % )                        |
| Embedded Multiplier 9-bit elements | 0 / 132 ( 0 % )                            |
| Total PLLs                         | 0 / 4 ( 0 % )                              |

PowerPlay Power Analyzer:

| PowerPlay Power Analyzer Summary       |  |
|--|--|
| PowerPlay Power Analyzer Status        | Successful - Tue Feb 17 21:36:43 2015            |
| Quartus II 64-Bit Version              | 14.1.0 Build 186 12/03/2014 SJ Web Edition       |
| Revision Name                          | proce  |
| Top-level Entity Name                  | proce  |
| Family                                 | Cyclone IV E                                     |
| Device                                 | EP4CE22F17C6                                     |
| Power Models                           | Final  |
| Total Thermal Power Dissipation        | 98.79 mW   |
| Core Dynamic Thermal Power Dissipation | 0.00 mW  |
| Core Static Thermal Power Dissipation  | 77.41 mW   |
| I/O Thermal Power Dissipation          | 21.38 mW   |
| Power Estimation Confidence            | Low: user provided insufficient toggle rate data |

RTL Viewer:

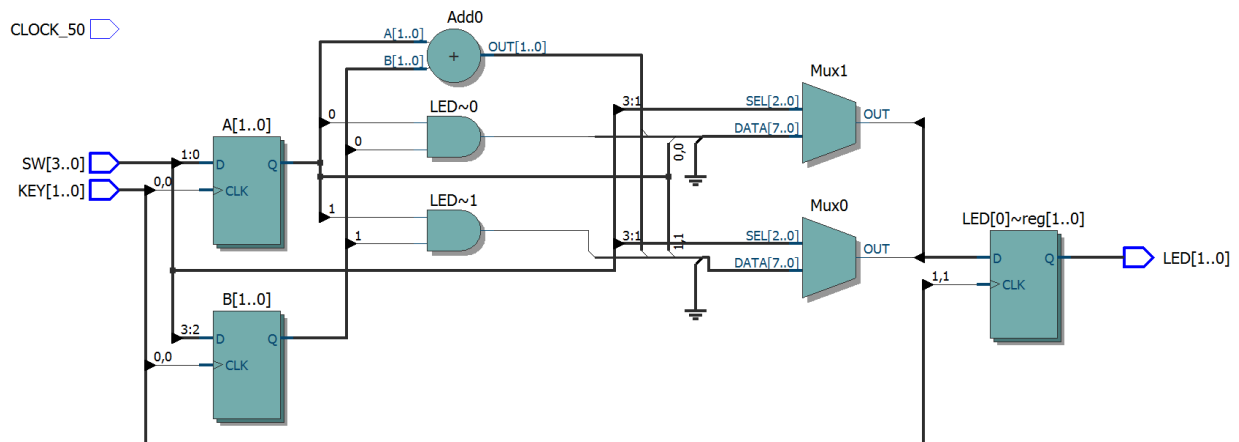

The output is in 2s-compliment (00 = 0, 01 = 1, 10 = -2, 11 = -1) and displays on 2 LEDs.

Here is a quick example of how this program works:

Flip switches 1 and 4.

Press KEY0 to store values, flip switches back.

Flip switch 3 (output A+B).

Press KEY1 to execute.

LED0 and LED1 light up.



## Appendix A (proce.v)

```
module proce(  
    input CLOCK_50,  
    input [3:0] SW,  
    input [1:0] KEY,  
    output reg [1:0] LED  
);  
  
    reg signed [1:0] A = 0;  
    reg signed [1:0] B = 0;  
  
    // load A and B when KEY[0] is pressed  
    always @(posedge KEY[0]) begin  
        A <= SW[1:0];  
        B <= SW[3:2];  
    end  
  
    // execute the instruction specified by the SW when KEY[1] is pressed  
    always @(posedge KEY[1]) begin  
        case (SW)  
            1: LED <= A;  
            2: LED <= ~A;  
            4: LED <= A + B;  
            8: LED <= A & B;  
            default: LED <= 2'bxx; // don't care if switch config is invalid  
        endcase  
    end  
  
endmodule
```